

a)  $P = I^2 R$  b)

$\sqrt{2} \quad 15W = I^2$

$\sqrt{12.3\Omega}$

$I = 1.1A$

b)  $\mathcal{E}_{mf} = I R_T = 14V$

$1.1(13.1)$

c)  $Q = It = 1.1 \times 60 = 66C$



$\frac{1}{R_{T,2}} = \frac{1}{R_1} + \frac{1}{R_3}$   $\frac{1}{20} + \frac{1}{36} R_{T,2} = 12\Omega$

$R_T = 32\Omega$

$I = \frac{V}{R_T} = \frac{3V}{32\Omega} = 0.094A$

$\sqrt{3} \quad V_1 = I R_1 = 1.875V$

$V_3 = 3V - 1.875 = 1.1V$

$I_3 = \frac{V_3}{R_3} = \frac{1.1V}{36\Omega} = 36mA$